



Everywhere Digital-Assisted High-Performance Analog-to-Digital Converter

Chi-Hang Chan, 陳知行 (Ivor)

State Key Laboratory of Analog and Mixed-Signal VLSI,
University of Macau, Macau, China



澳門大學
UNIVERSIDADE DE MACAU
UNIVERSITY OF MACAU



State Key Laboratory of
Analog and Mixed-Signal VLSI
模擬與混合信號超大規模集成電路
國家重點實驗室



IME
Institute of
Microelectronics
微電子研究院

Outline

- Motivations**
- Design Examples**
- Conclusion**




About Calibration

Engineering:
Calibration

In daily life (depend on the level) :
化妝 喬裝

Before Lite
Calibration



After Lite
Calibration

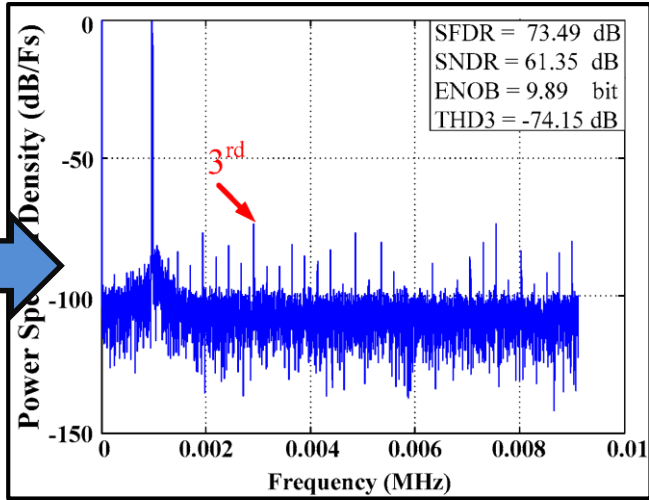  


About Calibration

Engineering:
Calibration

  In daily life (depend on the level) :
化妝 喬裝



Before Heavy
Calibration

 

After Heavy
Calibration




Digital-Assisted A/D

Digital-Assisted Solution:

- Effective for most of error in ADC
- Technology scaling friendly
- Preserve ADC integrity

Categorized in:

- Background
- Foreground

 


- With digital or analog /FB correction, sometime with analog-assisted

Digital-Assisted A/D

Considerations:

 
- Cost, including area, power, complexity and convergence
- Analog overhead (Auxiliary Channel, Additional DAC, etc.)
- Input constraints and others limitation on ADC (Loss DR, etc.)



- Need to consider calibration efficiency, necessity and testing


Outline

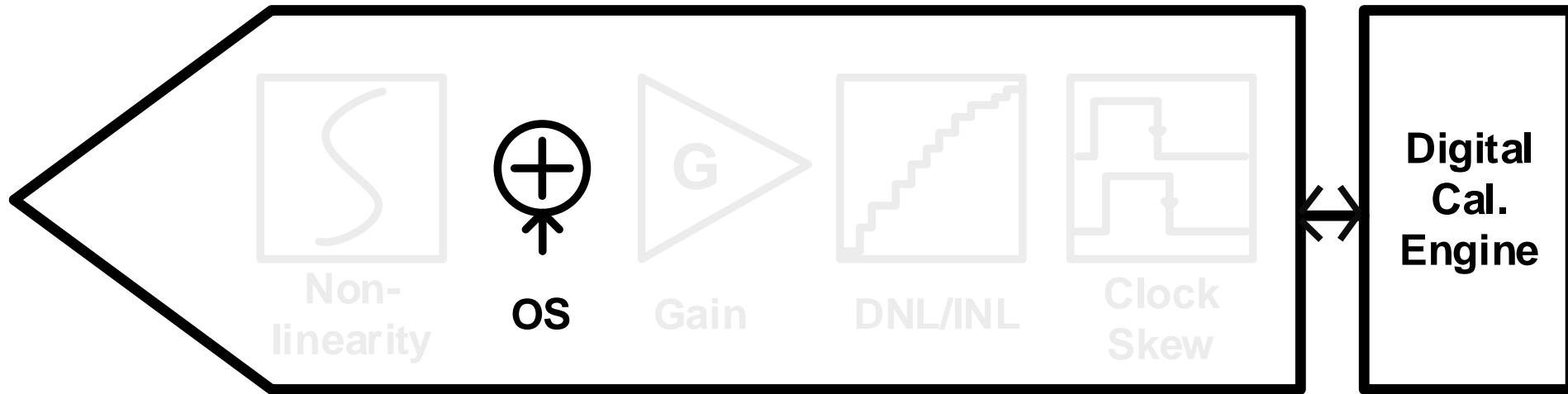- Motivations
- **Design Examples**
- Conclusion



SAR-Assisted Pipeline ADC with Background Offset Calibration

Offset in Pipeline-SAR ADCs




 


➤ **Offset mismatch between 2 stages from:**

- V_{os1} : First stage SAR
- $V_{os,ra}$: Residue amplifier
- V_{os2} : Second stage SAR



➤ **Can saturate the second stage input, must handle with analog feedback**

Second Stage Code Histogram

  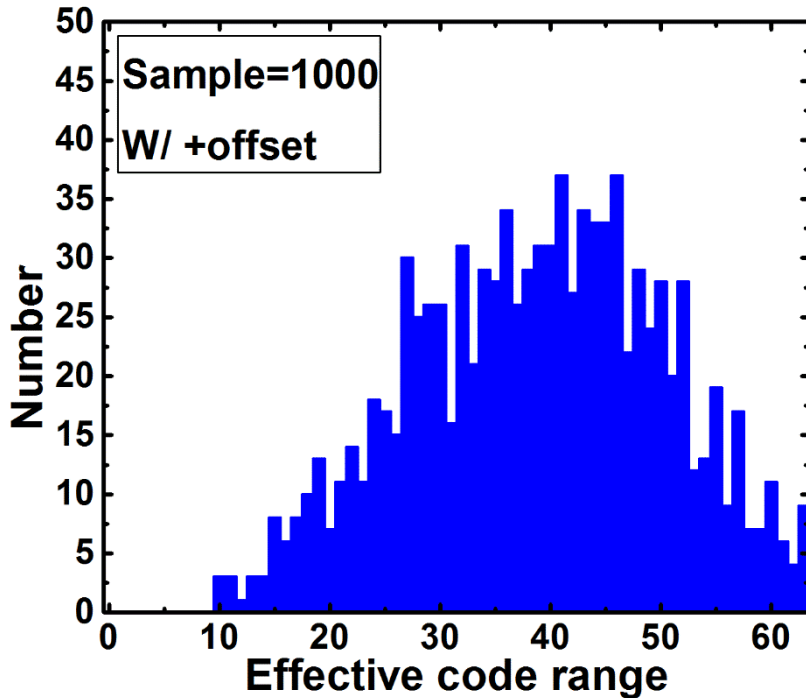 


- Code range is confined with the effective range when the offset is 0
- Code range varies with offset
- Code saturates by one side because of offset

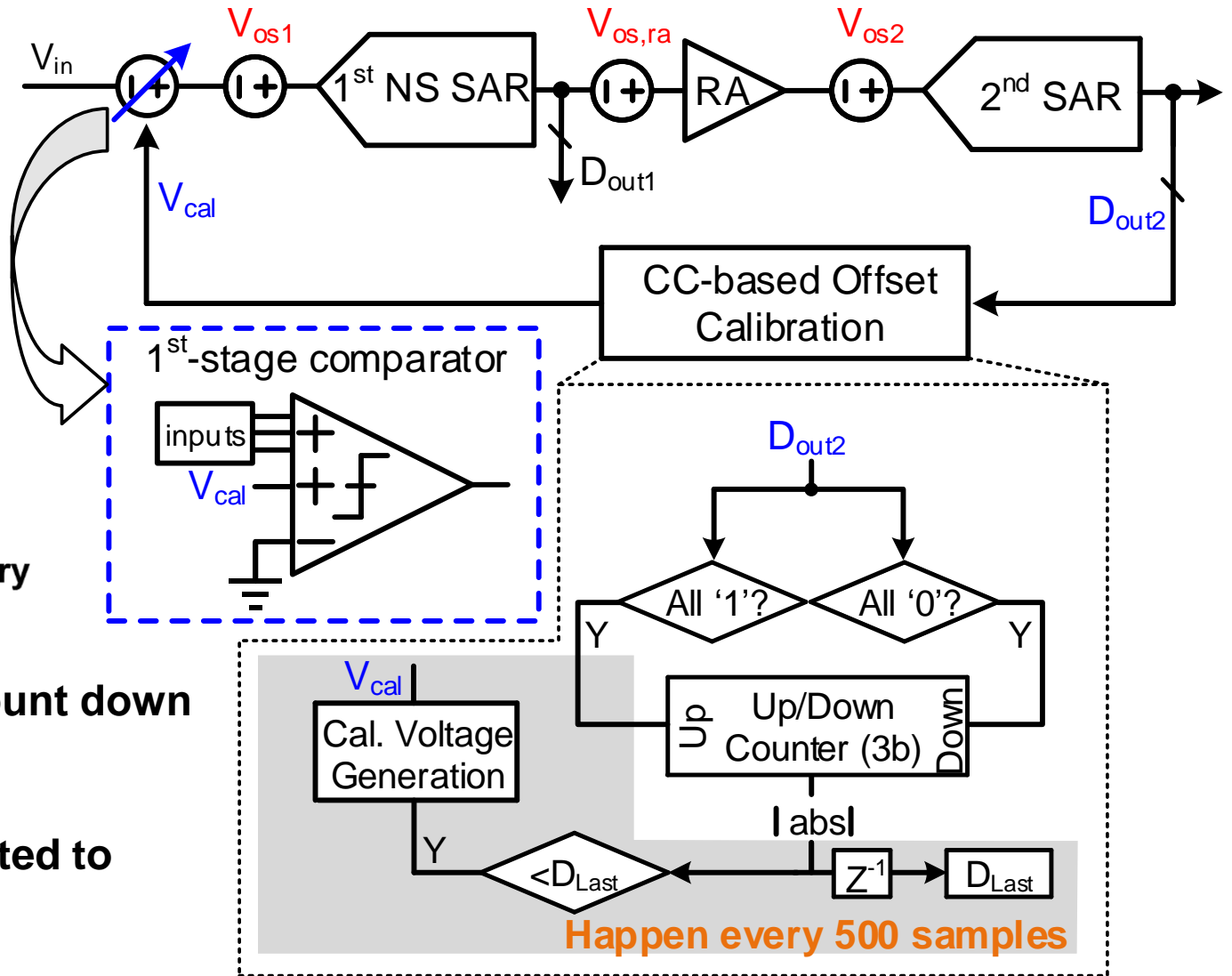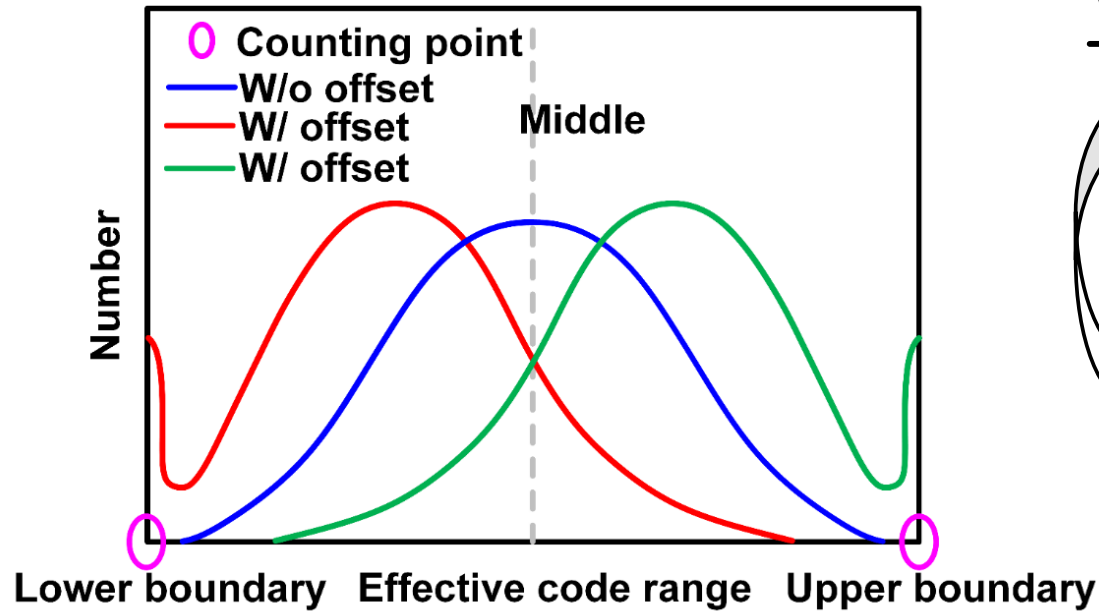Inter-stage Offset Calibration Scheme (1)




- D_{out2} equals to all '1', count up, vice versa count down
- The offset is calibrated on chip
- Convergence speed and accuracy are weighted to chose N

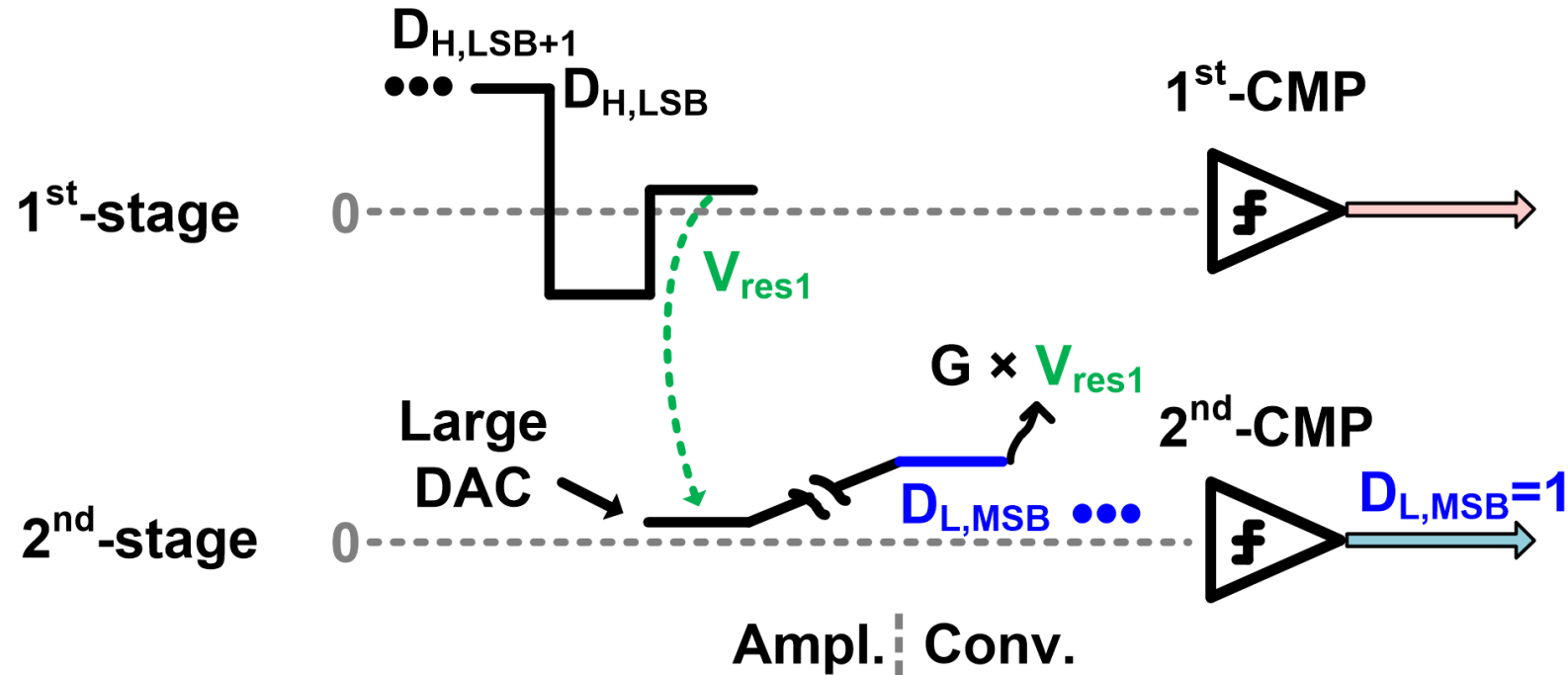Inter-stage Offset Calibration Scheme (2)




- No comparison needed for V_{res1} in conventional pipeline operation
- Sign of V_{res1} not change after amplification (**Utilize this redundancy?**)

Comparison of MASH 0-N and MASH N-0

 

- 1st-stage redundant comparison detects the sign of V_{res1}
- D_{res1} & $D_{L,MSB}$ should be the same without offset


Amplify Residue to the Next Stage

 

- Detecting the sign of overall offset voltage ($V_{os,in}$)


$$V_{os,in} = V_{os1} - \frac{1}{G} V_{os2}$$

Simplified ADC Schematic

 


- Same criteria for RA's offset detection
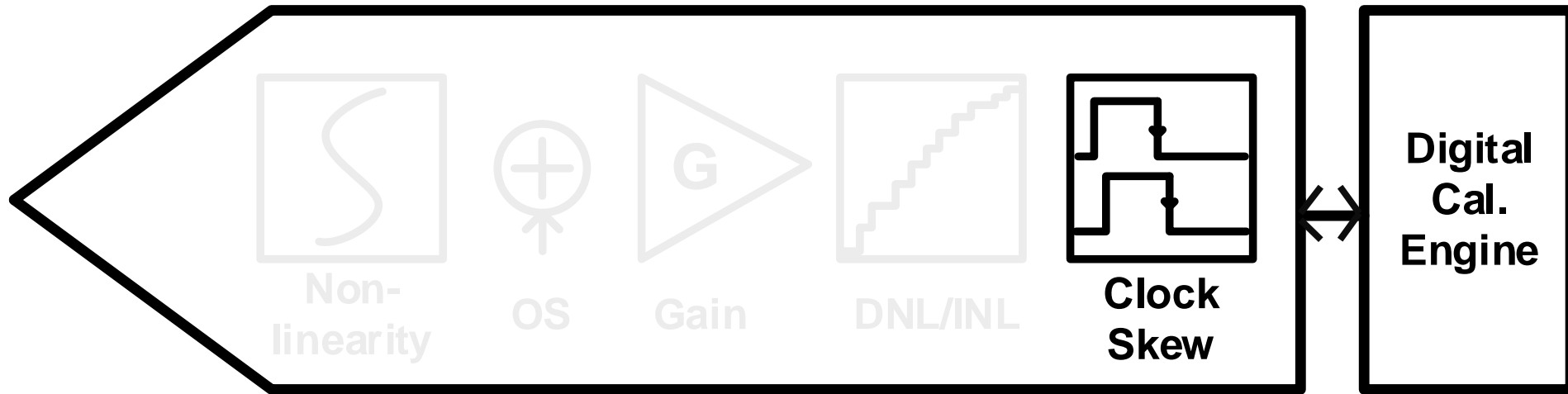
$$V_{os,in} = V_{os1} - \frac{1}{G} V_{os2} + \frac{1}{G} V_{os,RA}$$




**A 20GS/s 8b Time-Interleaved
Time Domain
ADC with Input-Independent Background
Timing Skew Calibration**

Timing Skew Mismatch

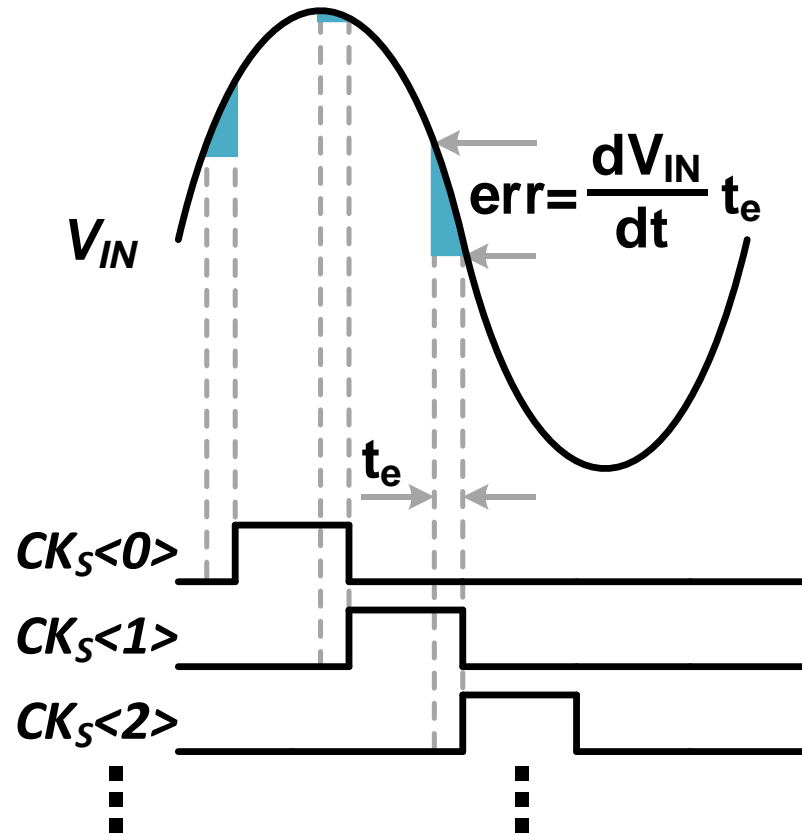

8x 8b 20GS/s TI-ADC Model

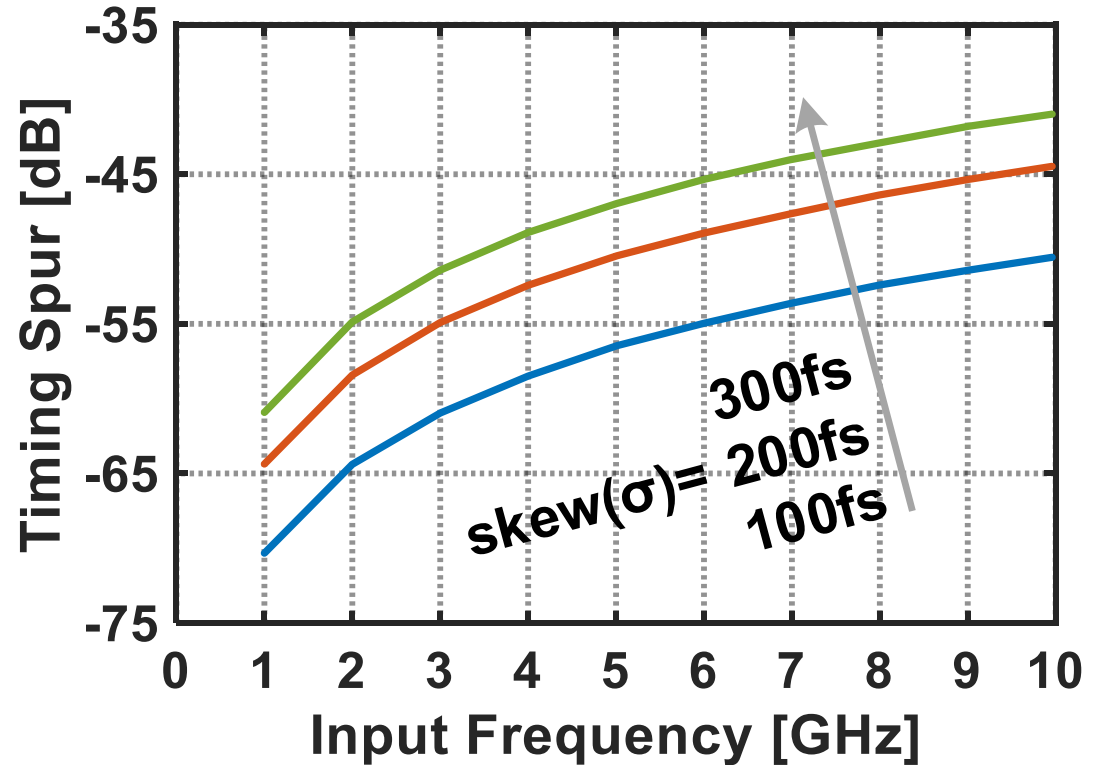


- For <-50 dB timing spurs with 10GHz input \rightarrow **skew(σ) < 100fs**

Prior Background Timing Skew Cal.

	N. Le Dortz ISSCC 14	B. Razavi JSSC 13	M. El-Chammas JSSC 11	S. Lee ISSCC 14
Type	All Digital Approach	Digital Estimation and Analog Feedback Control		
Estimation Methods	Derivative-based	Auto Correlation	Cross Correlation	Variance-based
Input Signal Limitation	Wide-Sense-Stationary & $<F_s/2$	Wide-Sense-Stationary	Busy Enough & Crossing Zero	Busy Enough & Large Swing
Extra Hardware	High-Speed Digital Filter	No	1-bit Reference ADC	Full-Speed Flash ADC

- All rely on certain input conditions


Objectives

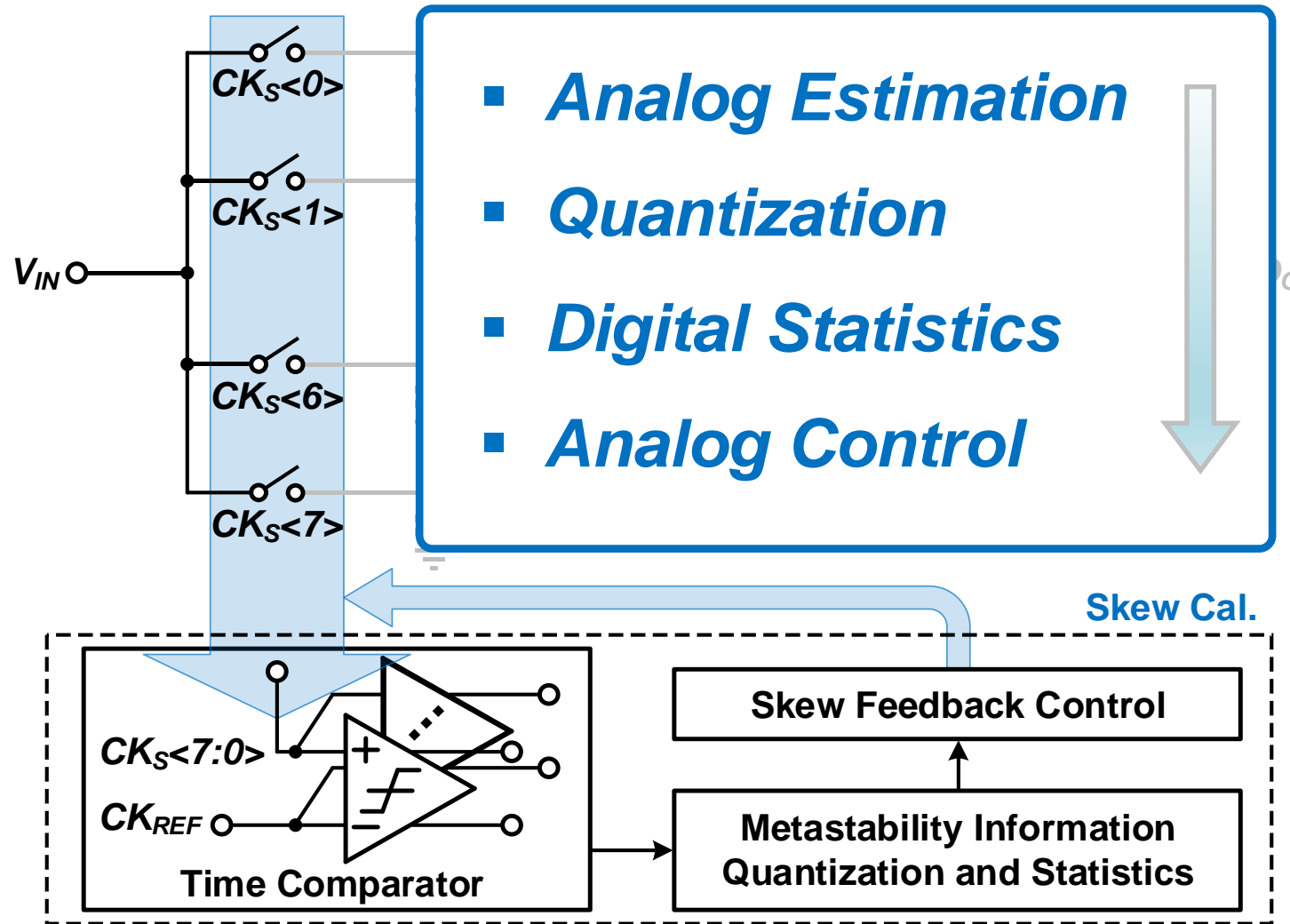


■ Timing Skew Cal.:

1. Does not rely on ADC input (background)
2. Does not base on A/D quantization
3. Remaining skew(σ) < 100fs
4. Small amount of iterations

Timing Skew Detection – (Skew < 0)

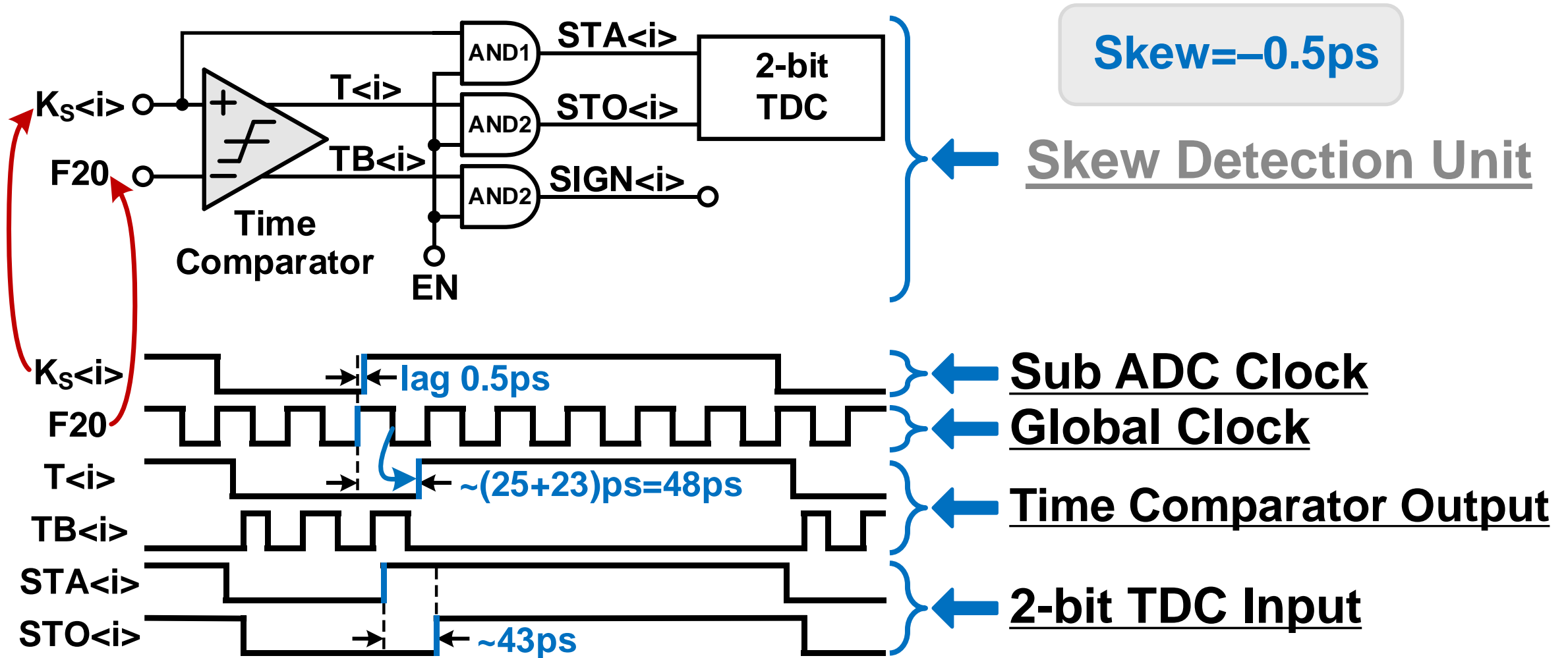


Detection T_{IN} vs. Timing Skew Value

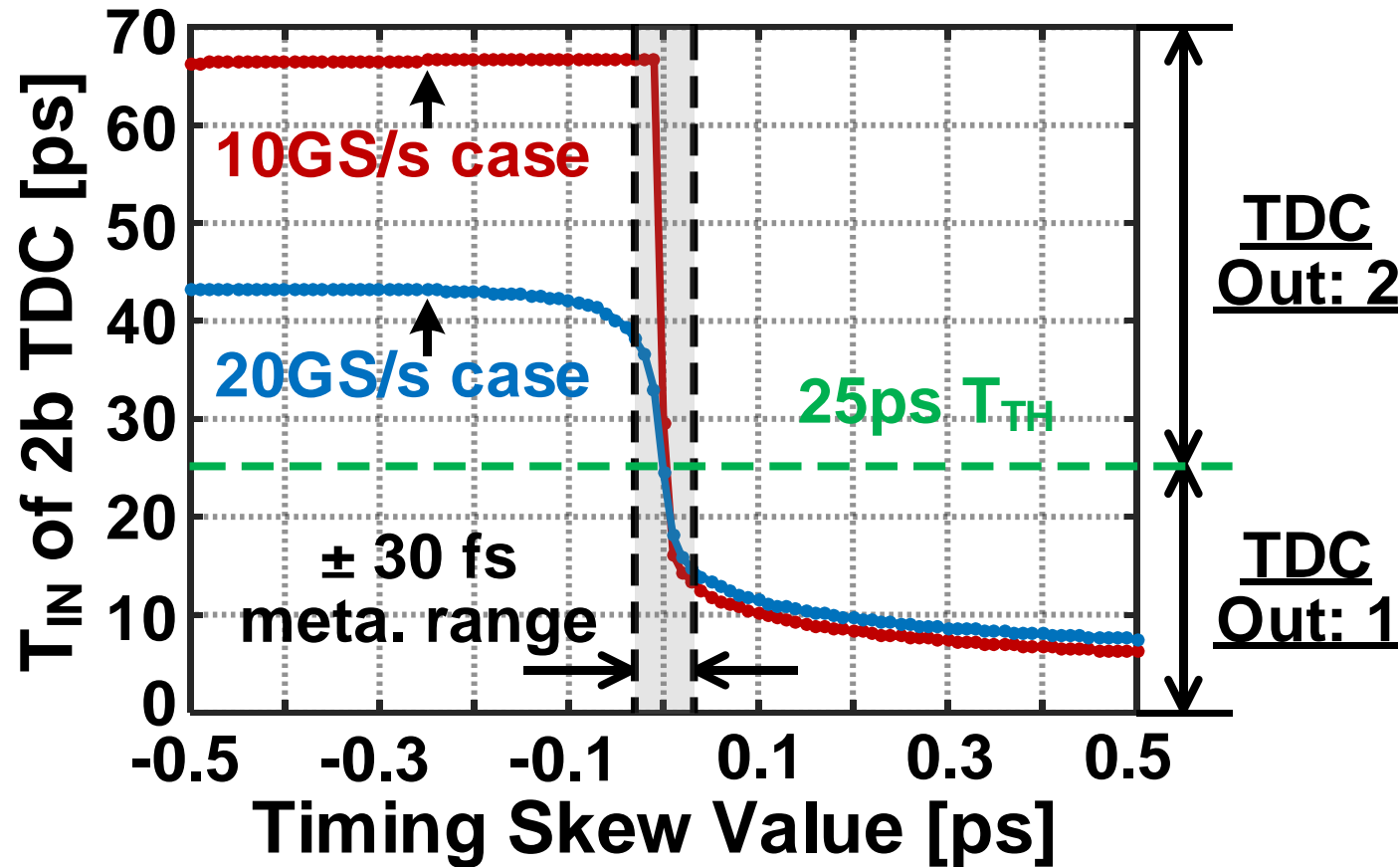


- **Quantization:**
→ 2b TDC ($T_{LSB}=25\text{ps}$)
- **Bound Accuracy:**
→ $\pm 30\text{fs}$ (meta. range)
- **Comparator Noise:**
→ 1k-sample statistics for one decision

Calibration – Time Comparator Offset

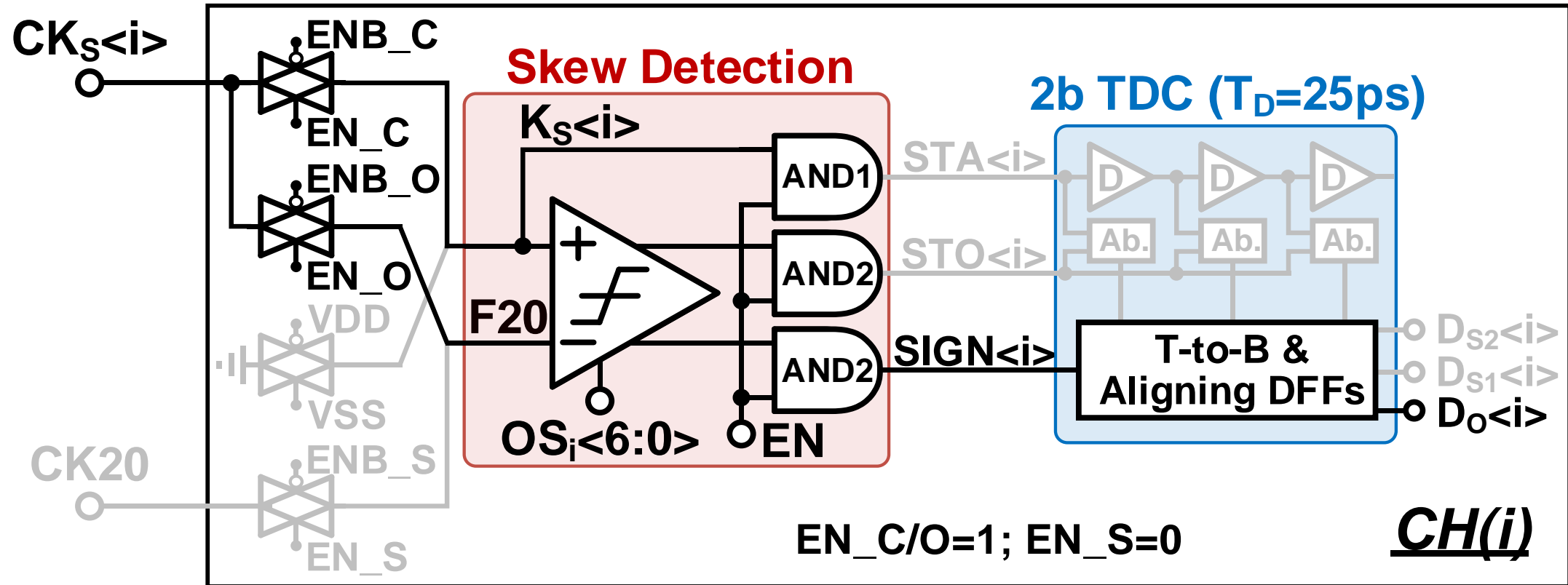

- Passive switches + 1k-sample statistics on $D_o<i>$

Calibration – Time Skew

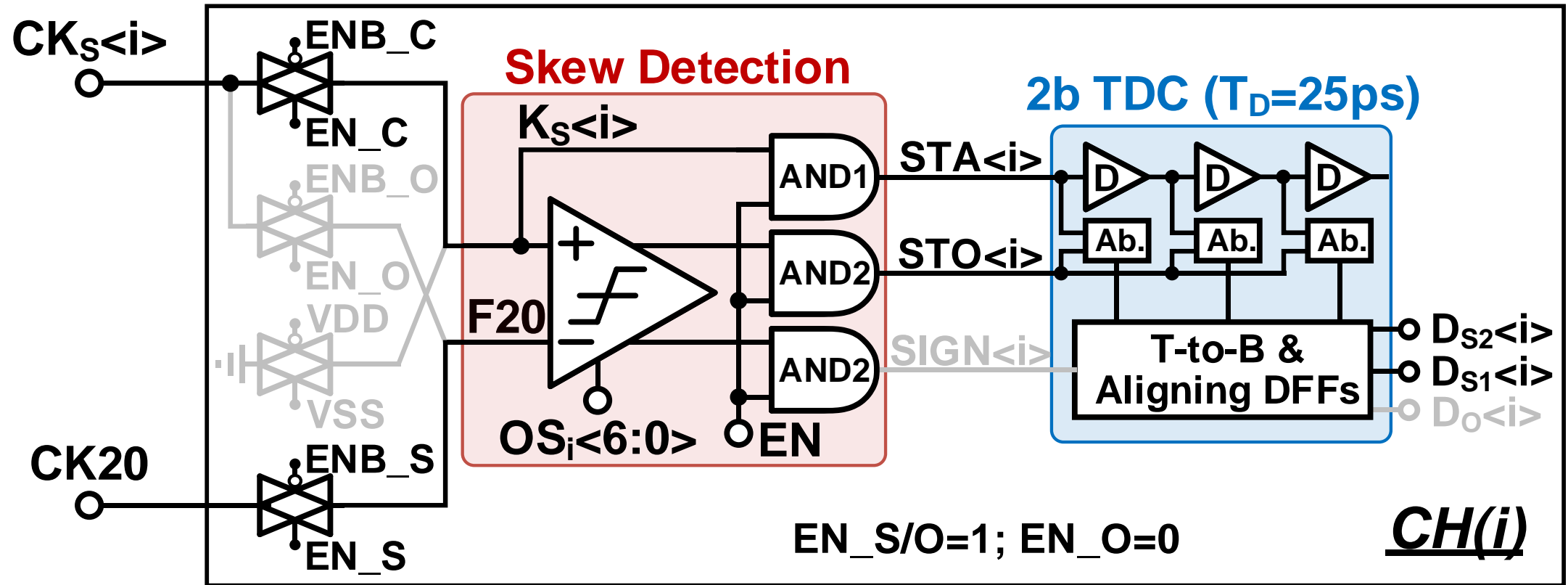

- Passive switches + 1k-sample statistics on $D_{S2}<i>$ & $D_{S1}<i>$

Timing Skew Calibration Comparison

	N. Le Dortz ISSCC 14	S. Lee ISSCC 14	B. Razavi JSSC 13	El-Chammas JSSC 11	V. H.-C. Chen ISSCC 14	This Work
Type	All Digital Approach	Digital Estimation and Analog Feedback Control			Analog Estimation and Analog Feedback Control	
Estimation Methods	Derivative-based	Variance-based	Auto Correlation	Cross Correlation	Build-in Cal Signal	Direct Timing Comparison
Unlimited Input Signal	X Wide-Sense- Sta. & $<F_s/2$	X Busy Enough & Large Swing	X Wide-Sense- Stationary	X Busy Enough & Crossing Zero	✓	✓
Constant Input Impedance	✓	✓	✓	X	X	✓
Timing Spur After Cal	-70dB @0.6GHz F_{IN}	-60dB @0.5GHz F_{IN}	-75dB @0.6GHz F_{IN}	-41dB @8.0GHz F_{IN}	-42dB @8.2GHz F_{IN}	-55dB @10GHz F_{IN}

Comparison


	This Work		S. Kim VLSI 20	B. Xu VLSI 16	V.H.-C. Chen ISSCC 14	Y. Frans VLSI 16
Architecture	TI-Time		TI-Time	TI-SAR/TDC	TI-Flash	TI-SAR
Technology	65nm CMOS		16nm FinFET	28nm CMOS	32nm SOI	16nm FinFET
Area [mm ²]	0.22		0.10	0.03	0.25	-
Channel Number	8x		16x	16x	8x	32x
Resolution [bits]	8		8	6	6	8
Supply [V]	1.0/1.2*	0.85/1.05*	0.9	0.85/0.95	0.9	0.9
Sampling [GS/s]	20	16	20	24	20	28
3dB-BW (GHz)	>16	>16	-	-	-	-
SNDR LF _{IN} [dB]	41.0	40.2	35.0	34.8	34.8	40.9
SNDR HF _{IN} [dB]	38.8	38.1	32.5	28.9	30.7	31.5
HF _{IN} [GHz]	10.0	8.0	1.0	11.9	10	14.0
Power [mW]	129.9	76.2	175.2	23.0	69.5	280.0
FoM _{LF} [fJ/conv.-step]	70.9	57.0	190.5	21.3	77.4	110.4
FoM _{HF} [fJ/conv.-step]	91.3	72.6	254.0	42.1	124.1	325.7

* Timing skew calibration works with a higher supply and 10% activation rate.

Time-Skew Calibration Measurement

- $F_{IN} = 9.974365$ GHz
- $F_S = 20$ GS/s

- Timing Spurs
- Harmonics (2nd-9th)

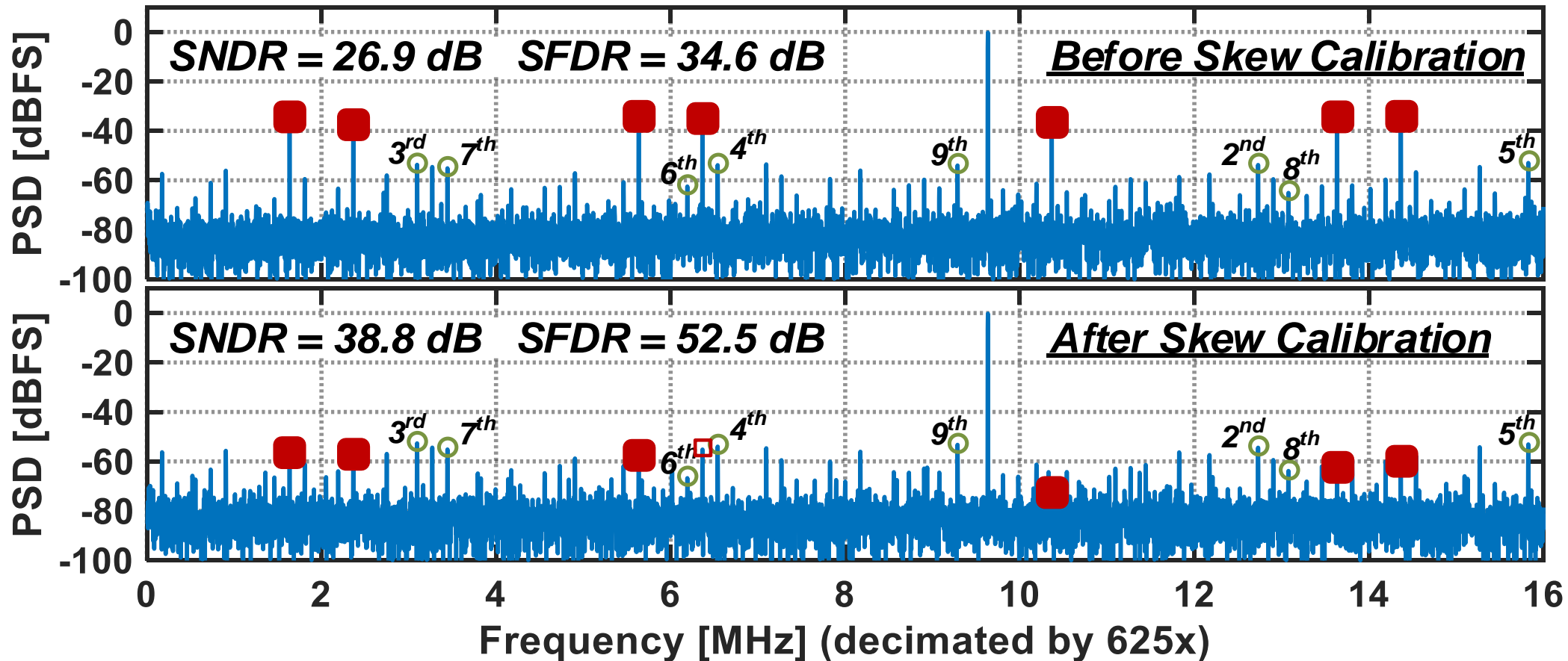


Timing
Spurs:

-34.6dB



-55.2dB

Bandwidth Measurement

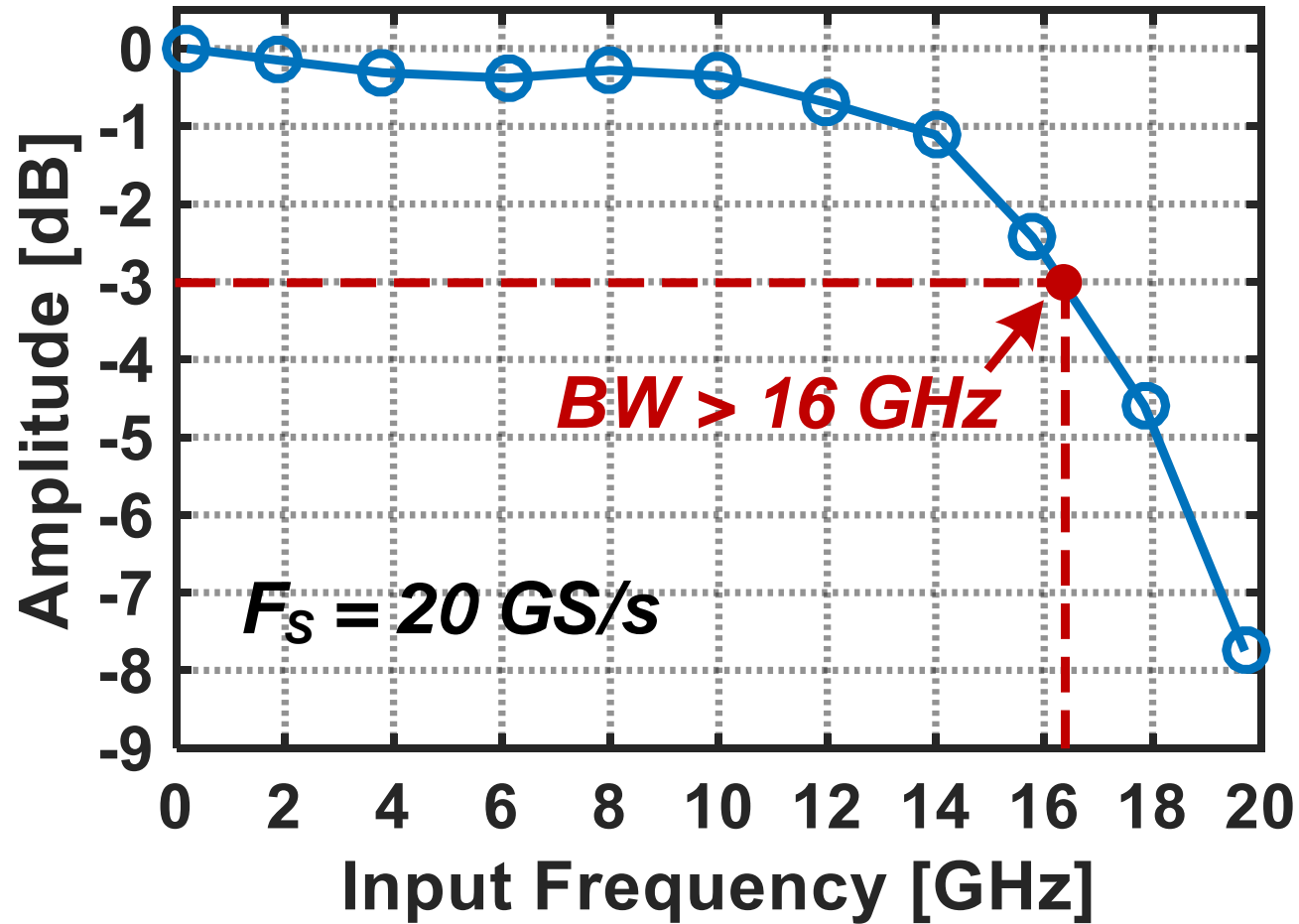

- Measured with input probe needle
- Benefit from inherent sub-channel buffer and 45-fF C_s

Outline


- Motivations
- Design Examples
- **Conclusion**

Future Works and Conclusion

- ❑ Many hybrid ADC architectures in recent year, how about calibration?**
- ❑ Analog-assisted is a good topic**
- ❑ Utilized concept from AI**
- ❑ Eventually, things are still fundamental, about ... cost**



 Hope you enjoy the workshop and my talk
Thank you for your Attention - Q&A



Thank you for your Attention
Q&A